

Race Around Condition

- The race around condition for J-K flip-flop, if $J=K=1$ and if $clk=1$ for a long period of time, the Q output will toggle as long as clk high which makes the output of the flip flop unstable or uncertain.
- This problem is called race around condition in J-K flip flop.
- Race Around Condition can be avoided by ensuring that the clock input is at logic "1" only for a very short time.
- This introduced the concept of Master Slave JK flip flop.

C	J	K
1	1	1

↳ toggling place occur.

• Methods to Remove Race Around Condition

Race condition can be removed in the following ways:-




(i) Increasing the delay of flip-flop

→ The Propagation delay should be made greater than the duration of clock pulse (T).

ie. $T/2 < \text{Propagation delay of flip flop}$

(But it is not good solution as increasing the delay will decrease the speed of the system.


(ii) Use of edge-triggered flip flop

(iii) Use of Master-Slave JK flip flop 

→ The race around condition can be removed with Master Slave JK flip flop.


Master-Slave JK Flip Flop

- The master-slave flip flop is constructed by combining two JK Flip Flop. These flip flops are connected in a series configuration.
- In these two flip flops, the 1st flip flop work as "master" called the master flip-flop. and the 2nd work as a "slave" called slave flip flop.
- The output from the master flip-flop is connected to the two inputs of the slave flip flop whose output is fed back to inputs of the master flip.
- And one circuit also includes as an inverter.
- In other words, If $C=0$ for a master flip flop, the $C=1$ for a slave fff. and if $C=1$ for master fff, then becomes 0 for

 

Block Diagram of :-
Master Slave JK Flip Flop

Logic Diagram

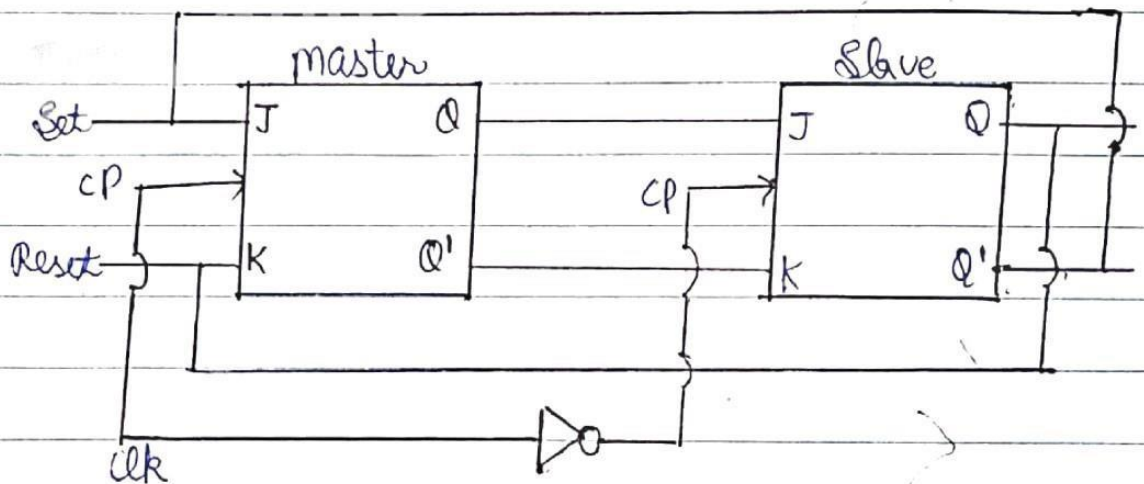

Master slave JK flip flop

When clock is low :-


- When the clock pulse (c) is 0, then slave flip-flop is enabled and master flip-flop is disabled.

The o/p of slave follows the o/p of master f/f, but during this time master f/f does not respond.

When clock is High:-

When the master is enabled and it follows the truth table of JK flip flop, but slave not respond.

Timing Diagram of a Master flip-flop

 

- When the clock pulse set to 1, the output of the master flip flop will be one until the clock input remains 0.
- The master flip flop is operational when the clock pulse is 1.
- The slave flip flop is operational when the clock pulse is 0.

* Applications of Flip-flops

- There are the various types of flip-flops being used in digital electronic circuits.
- The applications of flip-flops are as specified below :-

- ① Latch
- ② Counters
- ③ Data transfer
- ④ Data Storage
- ⑤ Registers
- ⑥ Memory
- ⑦ Shift - Registers
- ⑧ Storage - Registers
- ⑨ Sequence Generator.
- ⑩ Resisters.