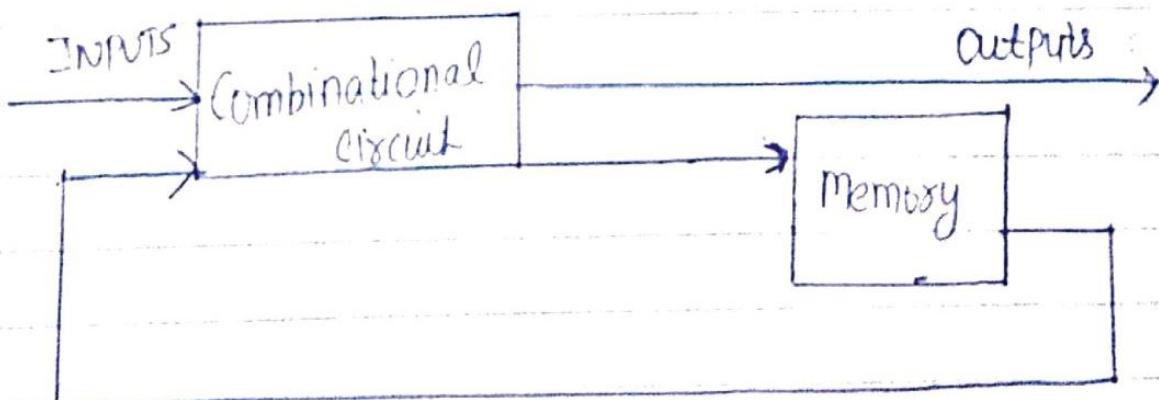


Sequential Logic Circuits

- The sequential circuit is a special type of circuit that has a series of inputs and outputs
- The output of the sequential circuits depend on both the combination of present inputs and previous output
- The Previous output is treated as the present state

formal definition :- In sequential circuits, the present output depends on the present input as well as past output/outputs.

Block Diagram :-



Types of Sequential Circuits

- Asynchronous sequential circuits
- Synchronous sequential circuits

Types of Sequential Circuits

Asynchronous Sequential circuit

Synchronous Sequential circuit

(i) Asynchronous Sequential circuit

- The sequential circuit whose output depends on the sequence in which the input changes is called asynchronous sequential circuit.
- In this type events can occur only after one event is completed - and there is no waiting for the timing pulse.
- The clock signals are not used in this. and
- The asynchronous circuit do not use clock pulses.

(ii) Synchronous Sequential circuit

In this, a clock pulse generator is used to provide regular timing pulses.

The output is change affect with respect to active transition of clock signal.