

An electronic circuit in which the output depends upon the present combination of the input.

Bittoo
TRADE MARK REGD.

Date: / /

Page/No.

Combinational circuits

combination of 2 or more logic gates is called combinational circuits.

6 types

① Half adder

② Full adder

③ Decoder

④ Encoder

⑤ Multiplexer

⑥ De Multiplexer

① Half Adder - It is used to add 2 bits/digits. It has 2 inputs and 2 outputs.

The first output is for sum (S)

The second output is for carry (C).

Q How 2 bits are added?

0	0	1	1
+ 0	+ 1	+ 0	+ 1
0 0	0 1	0 1	1 0
C S	C S	C S	C S


All four operations are done by the half adder.

(H.A)

It is made up of 2 logic gates

① XOR Gate

② AND Gate

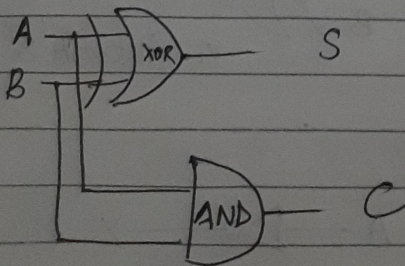

The working of half adder can be explained with the help of a truth table.

A	B	(XOR) S	(AND) C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logic eqⁿ for half adder.

$$\text{Sum} = A \oplus B = A'B + A.B'$$

$$\text{Carry} = A.B$$

(2) Full adder - It is used to add 2 binary numbers. It has 3 inputs and 2 outputs. The 3rd input is for carry generated by the previous digits.



It is made up of

- ↓ ↓ ↓
 ① XOR gate ② AND gate ③ OR gate.

Here, $S = A \oplus B \oplus C$

$$C = AB + BC + AC$$

$$C = (A \oplus B).C + A.B$$

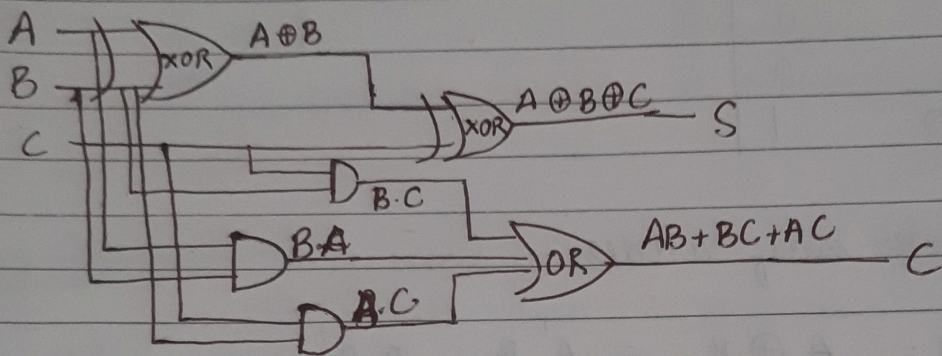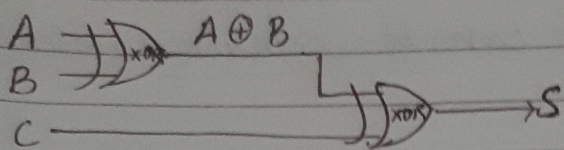

The working of full adder can be explained using its truth table.

A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Parallel Adder - It is a combination of various full adders.

for ex. 4 bit parallel adder has 4 full adders.

A ₁	A ₂	A ₃	A ₄
1	1	0	1
B ₁	B ₂	B ₃	B ₄
1	0	1	1

③ Decoder - It is a combinational circuit that converts binary digits into equivalent decimal numbers.

In other words it converts 'n' binary digits into equivalent decimal codes.

It may have n inputs and 2^n outputs.

Ex: Let us have $n=3$ inputs, then we have $2^3 = 8$ outputs

Such a decoder is known as 3 to 8 line decoder

ie: n to 2^n line decoder



I_1	I_2	I_3	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

De-Morgan's Theorem - used while dealing with NOR and NAND gates.



proof $(x+y)' = x'y' \Rightarrow$ NOR gate

$(xy)' = x'+y' \Rightarrow$ NAND gate.


NOR Gate

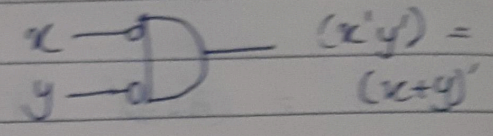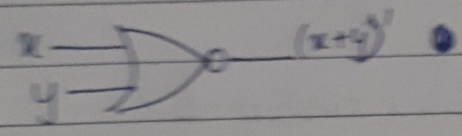

NAND Gate

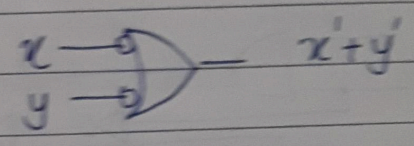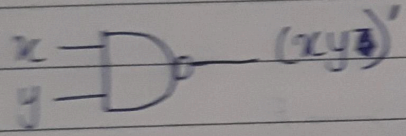


$F = ABC + ABC' + A'C$

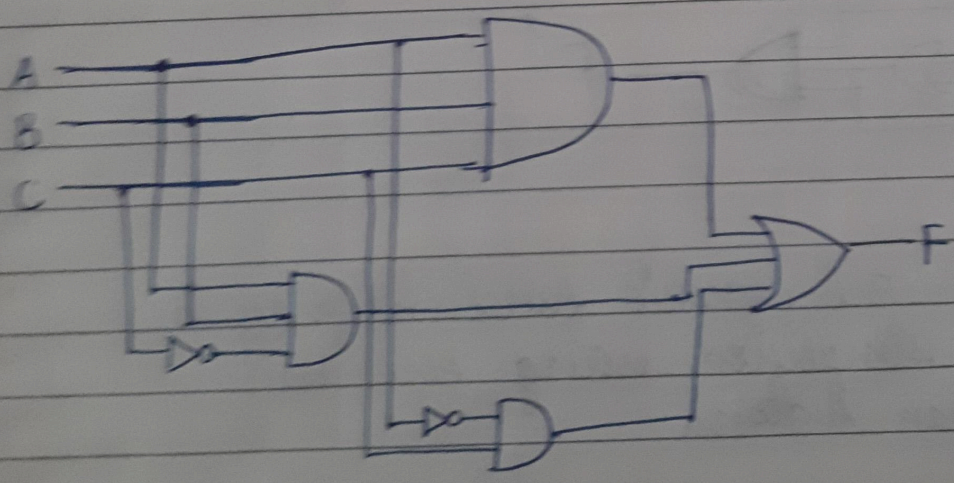

F can be represented as



$$F = AB(C+C') + A'C$$
$$= AB + A'C$$

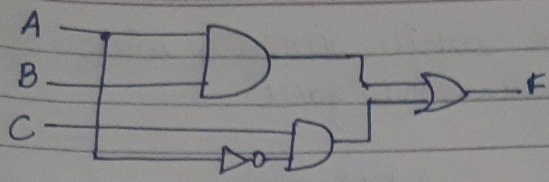

Complement of a Function

When $F = AB + C'D + B'D$

$$F' = (A+B)' (A'+B') (C+D) (B+D)'$$

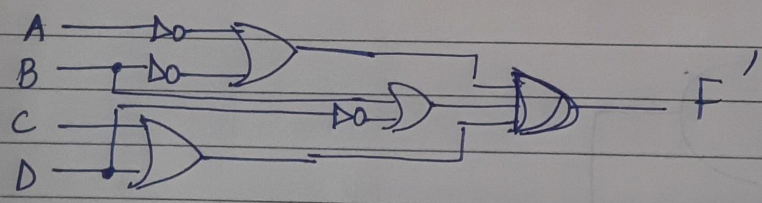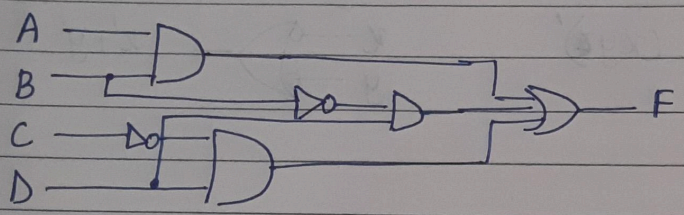

Map Simplification. The algebraic functions may be simplified using the basic relations of Boolean Algebra.


The map-method is regarded as a pictorial arrangement of the truth table.

This method is also known as the k-map or Karnaugh map.

Combinational Circuits

A combinational circuit is a connected arrangement of logic gates with a set of inputs and outputs.

Block diagram.

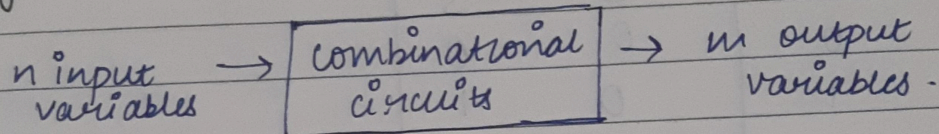


Combinational circuit can be described by a truth table showing the binary relationship b/w the n input variables and the m output variables.

Half Adder A combinational circuit that performs the arithmetic addition of 2 bits.

Truth table:

x	y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logic diagram:

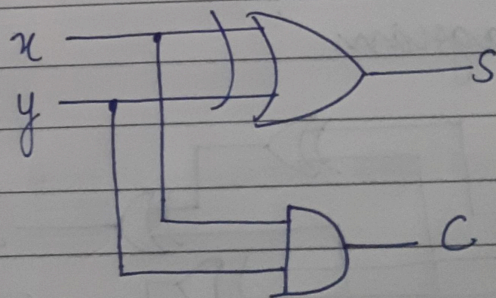

Boolean functions:

$$S = x'y + xy' = x \oplus y$$

$$C = xy$$


XOR ~~AND~~ gate.

AND gate

Combinational Circuits

A combinational circuit is a connected arrangement of logic gates with a set of inputs and outputs.

Block diagram.

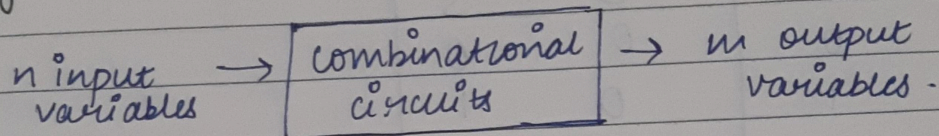


Combinational circuit can be described by a truth table showing the binary relationship b/w the n input variables and the m output variables.

Half Adder A combinational circuit that performs the arithmetic addition of 2 bits.

Truth table:

x	y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logic diagram:

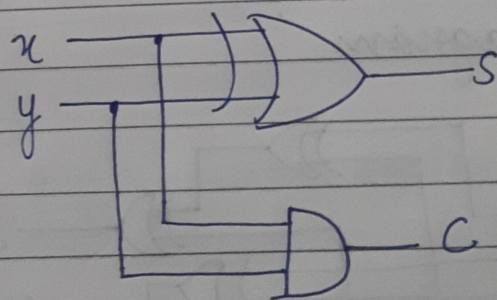

Boolean functions:

$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

XOR gate


AND gate

Parallel Adder It is a combination of various full adders.

A 4 bit 11 adder has 4 full adders

ex.
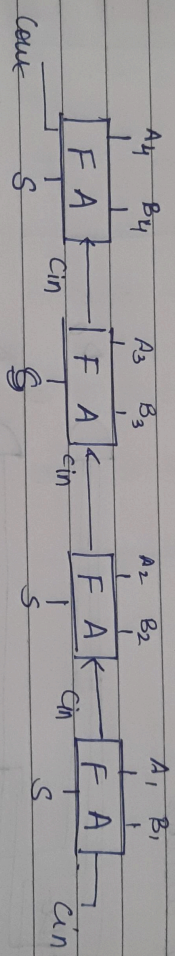
$$\begin{array}{r}
 1A_1 \quad 1A_2 \quad 0A_3 \quad 1A_4 \\
 + 1B_1 \quad 1B_2 \quad 0B_3 \quad 0B_4 \\
 \hline
 11011
 \end{array}$$



Decoder It is a combinational circuit that converts binary digits into equivalent decimal numbers.

It converts n binary digits into equivalent decimal codes.

They have n inputs and 2ⁿ outputs.


if we have 3 inputs, we get 8 outputs

such a decoder is known as 3 to 8 line decoder

Truth table:

A	B	C	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	0	0
0	1	0	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0

logic circuit -

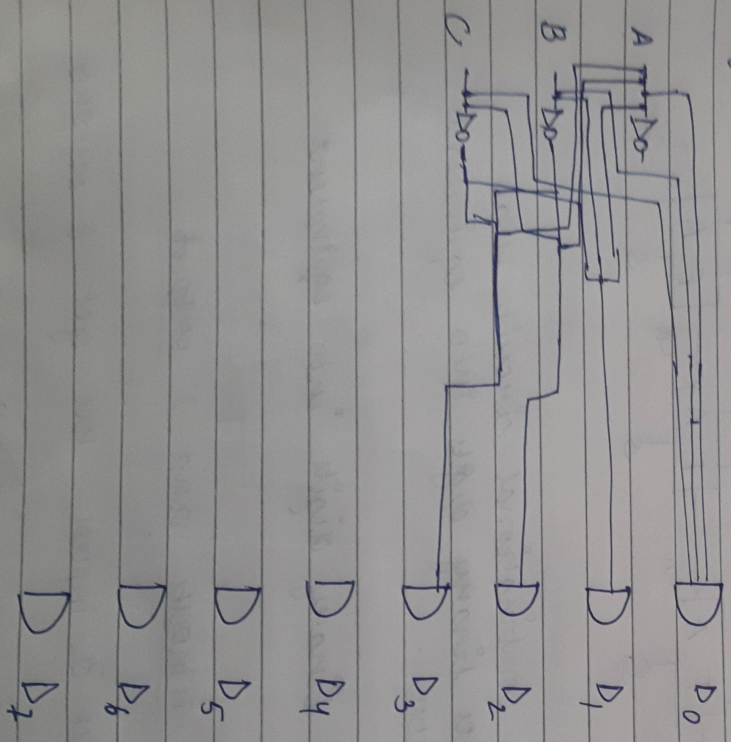


De-Multiplexer - It is a combinational circuit in which input is divided into 1 to 2^n output where n is the number of selection lines.

If there are 2 to selection lines, i.e. $n=2$, there will be 4 outputs.

Such a de-multiplexer (De-mux) is known as 1 to 4 de mux

F	S_0	S_1	D_0	D_1	D_2	D_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

logic circuit

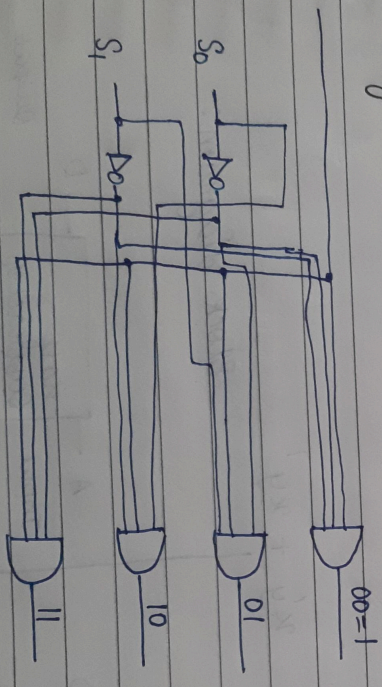

$$0 = a'$$

$$1 = a$$

Half Subtractors

1	0	1	0
- 1	- 0	- 0	- 1
0	0	0	1
B	D	B	D

X	Y	D	B
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0

$$x' y$$

XOR Gate

logic eqⁿ



$$x' = 0 \quad x = 1$$

$$D: \quad x \oplus y = x'y + xy'$$


$$B: \quad x'y$$

Block diagram:

logic circuit:

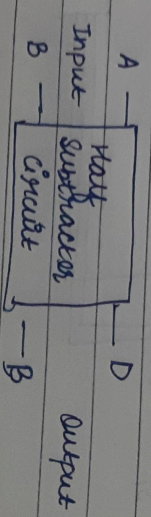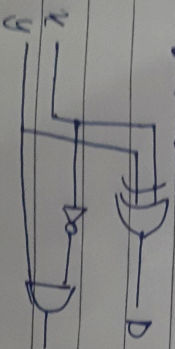

Full Subtractor

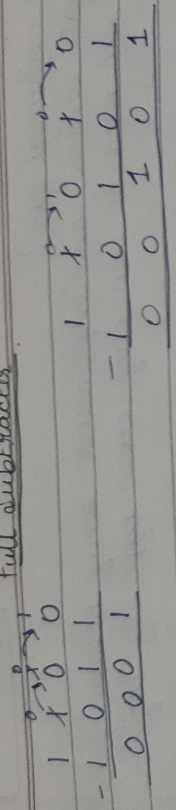

Logic Truth Table

Input			Output	
A	B	Borrow in	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Logic eqⁿ

$$D = A \oplus B \oplus B_{in}$$

$$B_{out} = A'BC + A'BC' + A'BC + ABC$$

$$= A'(BC + BC') + (A'+A)BC$$

$$= A'(B \oplus C) + BC$$

