

Don't have conditions. Minimums that may produce either 0 or 1 for the function are said to be don't care conditions and are marked with an 'x' on the map.

It is a condition in which we can allocate a non occupied cell, a value x to make lesser numbers of groups. The value of x may be 0 or 1.





x here is don't care and can be supposed as 0 or 1.

Combinational circuit is a connected arrangement of logic gates with a set of inputs and outputs.

The n binary input variables come from an external source, the m binary output variables go to an external destination. If the there is an interconnection of logic gates.

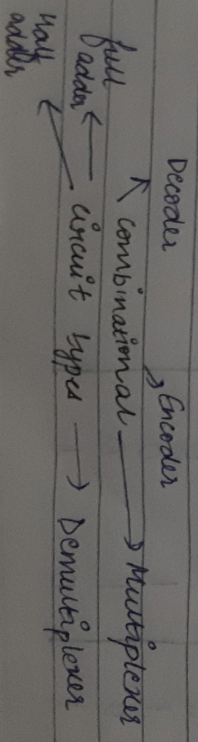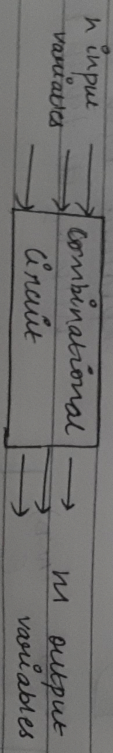A combinational circuit transforms binary info from the input data to the required output data.



X

Half Adder The combinational circuit that performs the arithmetic ~~circuit~~ is addition of two bits is called a half adder. It has 2 inputs and 2 outputs. The first output is for sum (S) and the second output is for carry (C)


Q How are 2 bits added in a computer?

0	0	1	1
+ 0	+ 1	+ 0	+ 1
0 0	0 1	0 1	1 0
C S	C S	C S	C S

All 4 operations are done by half adder

It has 2 gates

- ① XOR
- ② AND

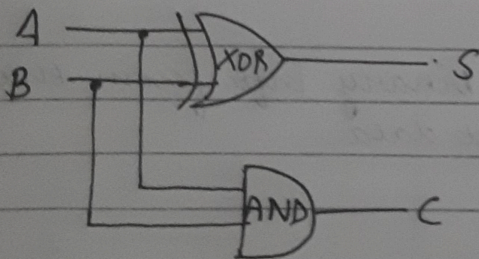

The working of half adder can be explained with the help of its truth table

A	B	(XOR) S	(AND) C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logic eqⁿ for half adder:

$$\text{Sum} = A \oplus B = A'B + AB'$$


$$\text{Carry} = A \cdot B$$

Full Adder is a combinational circuit that forms the arithmetic sum of 3 input digits.

It has 3 inputs and 2 outputs.

The third input is for carry generated by the previous digits.

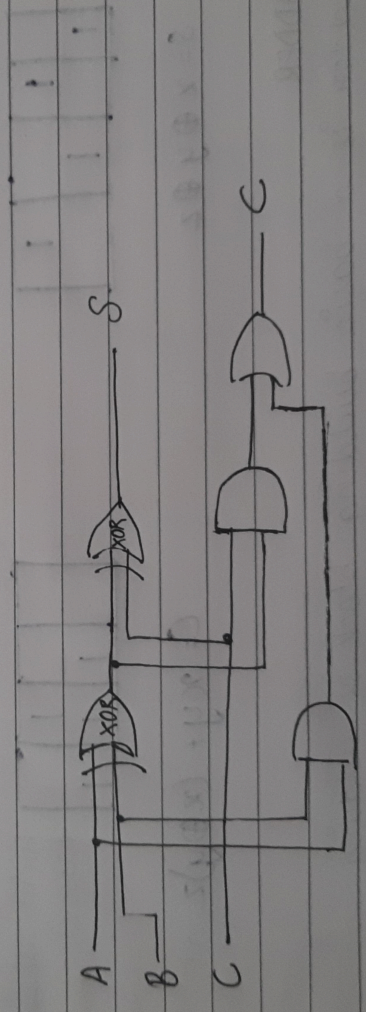It has ~~2~~ ² XOR gates, ~~2~~ ² AND gates and 1 OR gate.



Logic eqⁿ for full adder


$$S = x \oplus y \oplus z$$

$$C = xy + (x \oplus y)z \quad [xy + yz + xz]$$


The truth table for full adder is:

A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Map for full adder:

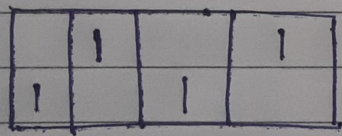

$$S = x \oplus y \oplus z$$

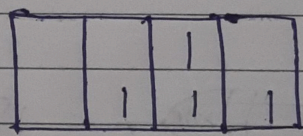


$$C = xy + (x \oplus y)z$$

HALF ADDER

Half adder is a basic building block of adding 2 numbers at 2 inputs and produce out 2 outputs. The adder is used to perform OR operation of 2 single bit binary numbers.

Block diagram

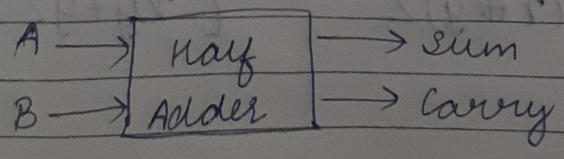

Truth Table


Inputs		Outputs	
A	B	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Logic eqⁿ
 $S = x'y + xy'$
 $C = x \cdot y$

Half Adder

~~AND~~ AND Gate
 XOR Gate

Logical circuit

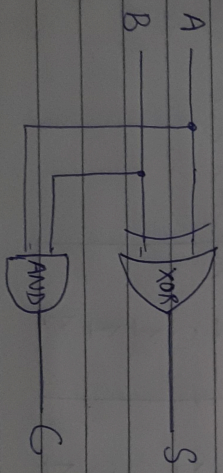


FULL ADDER

The Full adder is used to add three 1-bit binary numbers, A, B and carry C.

The full adder has 3 input states and 2 output states. i.e. Sum and carry.

Block Diagram

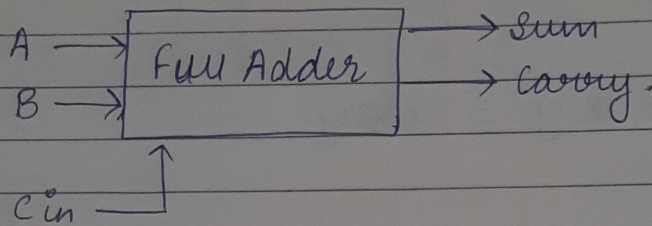

Truth Table


Inputs			Outputs	
A	B	Cin	sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- A and B are the input variables. These are the 2 significant bits that will be added.
- C_{in} is the third input which represents the carry, which is fetched from the previous lower significant position.

logic eqⁿ.

$$S = xy' + x'y + xy' + xy = x \oplus y$$
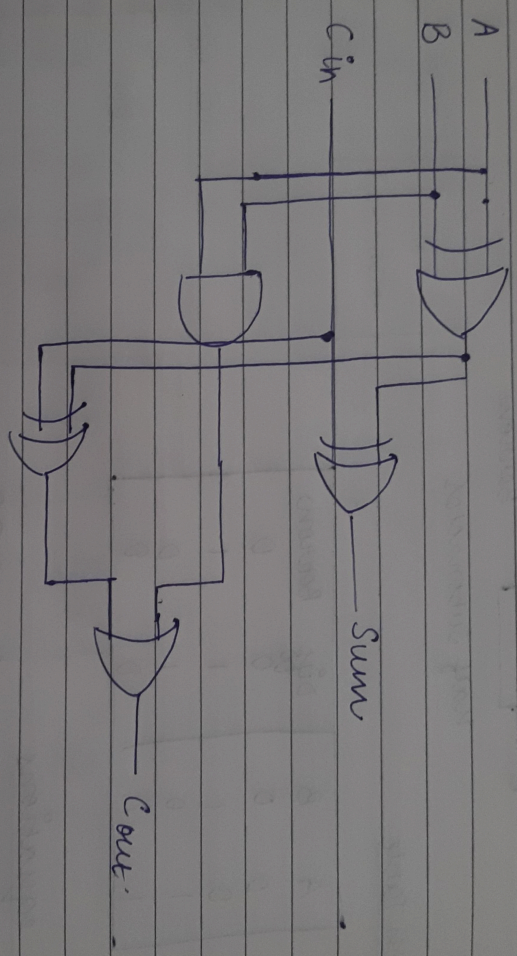
$$C = xy + yz + zx \text{ or } xy + z(xy)$$



HALF SUBTRACTOR

Half subtractor is a digital logic circuit that performs binary subtraction of two single bit binary numbers. It has 2 inputs, A and B, and two outputs, Difference and Borrow.

2 gates


↳ XOR and NOT gates.

D = XOR gate.

B = NOT gate.

Half subtractor is a combination circuit with 2 inputs and 2 outputs difference and borrow.

Block Diagram

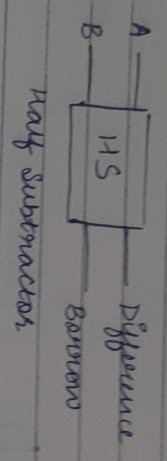

Truth Table


A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

logic equations

$$D = A \oplus B$$

$$B = A'B$$


logic diagram

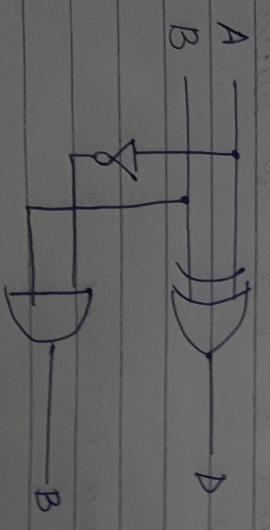

Full Subtractor

A full subtractor is a combinational circuit that performs subtraction of 2 numbers. It has 3 inputs and 2 outputs. Borrow in and Diff.

Block diagram

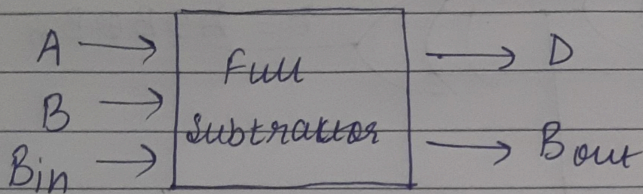

Truth Table

Input			Output	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = A'B'Bin + A'B \cdot Bin' + A B' Bin + A B Bin$$


$$Bout = A'B Bin + A'B Bin' + A'B' Bin + A \cdot B \cdot Bin$$

Logic eqⁿ :

$$D = (A \oplus B) \oplus B_{in}$$


$$B_{out} = A' B_{in} + A' B + B B_{in} = (A \oplus B)' \cdot B_{in} + A' B$$

Logic diagram :

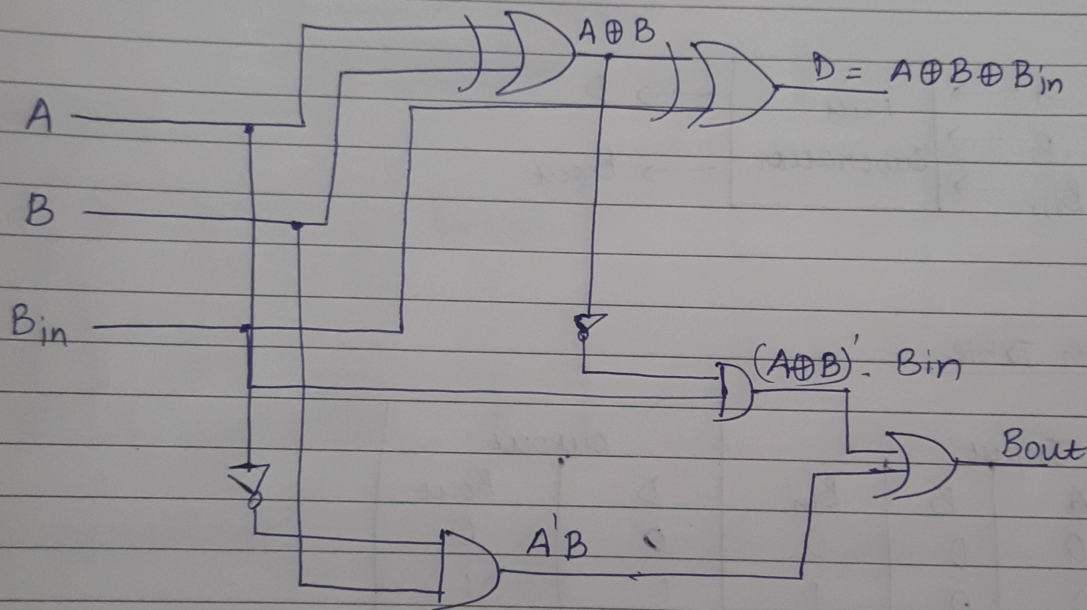


ENCODER. Encoder is a digital circuit that converts a set of binary inputs into a unique binary code.

It has 2^n input lines and n output lines.

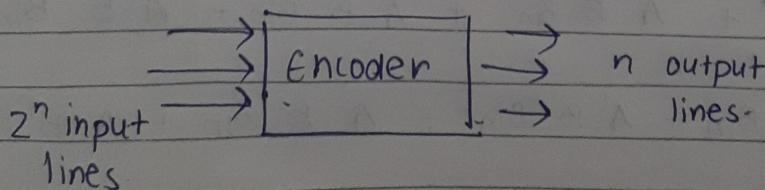

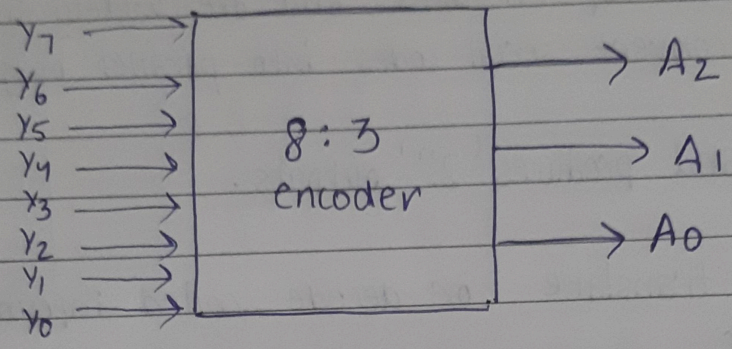example 8:3 encoder [octal to binary]

8 inputs Y_7 to Y_0 and 3 outputs A_2, A_1 and A_0



Truth table for 8 to 3 line encoder

INPUTS								OUTPUTS		
Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

logic eqⁿ

$$A_2 = Y_7 + Y_6 + Y_5 + Y_4$$

$$A_1 = Y_7 + Y_6 + Y_3 + Y_2$$

$$A_0 = Y_7 + Y_5 + Y_3 + Y_1$$

Decoder. A binary decoder is a digital circuit that converts a binary code into a set of outputs.


Decoders are the inverse of encoders and are widely used in digital systems to convert serial codes into parallel outputs.

It has 'n' inputs and produces ' 2^n ' outputs.

'Decoder' means to translate or decode coded information from one format to another.

A digital decoder transforms a set of digital input signals into an equivalent decimal code at its output.

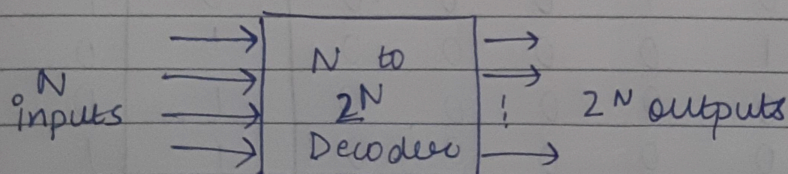
⇒ A **decoder** is a **combinational circuit** that converts binary information from **n input lines** to a maximum of **2^n unique output lines**.



for ex:

A binary decoder that has 2 inputs ~~have~~ has $2^2 = 4$ outputs - and it is called


2-to-4 line binary decoder.

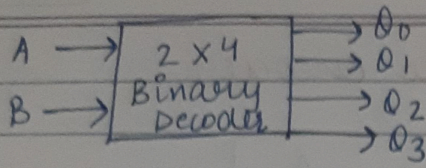

Truth Table for 2 to 4 line decoder:

A	B	Q ₀	Q ₁	Q ₂	Q ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

logic circuit for 2 to 4 line decoder

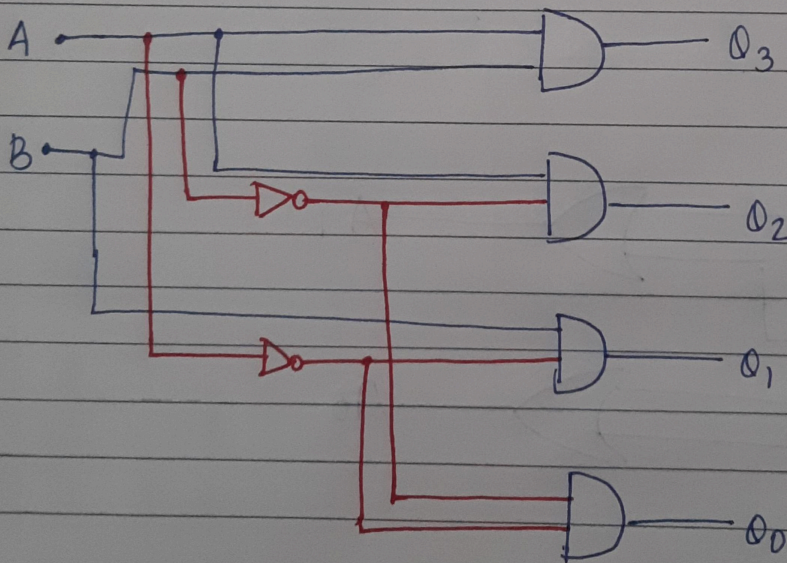

logic eqⁿ:

$$Y_3 = A_1 \cdot A_0$$

$$Y_1 = A_1' \cdot A_0 \cdot B$$

$$Y_2 = A_1 \cdot A_0'$$

$$Y_0 = A_1' \cdot A_0'$$

$$A \cdot B$$

$$A' \cdot B'$$

Truth Table for 4 to 2 line encoder

Y_3	Y_2	Y_1	Y_0	A_1	A_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Logic equations:

$$A_1 = Y_3 + Y_2$$

$$A_0 = Y_3 + Y_1$$

Logic circuit:

