

Combinational

Output of CC is entirely dependent on its inputs

They are ready to use, and there is no need to control them

ex: full adder, half adder, decoder, encoder, mux, de-mux

Sequential

Output of SC also depends on the clock pulse as well as the storage elements.

They are controlled by the clock pulse

ex: flip-flop, registers, counters.

Sequential circuits - are combination of logic gates, clock pulse and storage elements -

Flip Flop. The storage elements ^{required} employed in by sequential ~~elem~~ circuits are called flip flops. It has 2 states on and off.

They are bistable devices that store 1 bit of information at a time. (0 or 1)

They have some inputs, a clock pulse and an output.

Commonly used flip flops:


- ① SR ② JK ③ D ④ T ⑤ master-slave

① SR flip flop

It has 2 inputs S (set) and R (reset) and 2 outputs Q and Q'.

S is for 1 and R is for 0.

Block diagram for SR flip flop is

 

Working of SR flip flop can be explained with the help of its truth table.


S	R	Q next
0	0	no change
0	1	reset (0)
1	0	set (1)
1	1	? Indeterminate

↓
This drawback is called Race condition

When both inputs S and R are high (1) then, this flip flop does not give a certain output. This is called indeterminate state. It happens because both inputs are high and there is a race between them. Hence, it is called race condition

This problem is solved by JK Flip Flop.

Logic circuit

 


② JK Flip Flop.

Invented (revised) by Jack Kinby

It has 2 inputs J and K and 2 outputs as well.



Block diagram for JK flip flop is:

 


The working of JK flip flop can be explained with the help of its truth table.

J	K	Q next
0	0	no change
0	1	reset (0)
1	0	set (1)
1	1	$Q'(t)$

↓
complement of the present state

  

 
③ D flip flop It is obtained from the SR flip flop.



The D flip flop can be obtained by combining S and R inputs into a single input with the help of NOT Gate


It has 1 input named D so there will only be 2 combinations in the truth table

D	Output
0	Reset (0)
1	Set (1)

 

This cross connⁿ is called LATCH

 ④ T flip flop It is obtained from JK flip flop
 Can be obtained by combining the J and K inputs into one input




Truth Table.

T	Output
0	no change
1	0' (+)

↳ complement of present state

T → Toggle

 


⑤ Master Slave flip flop

It is a combination of 2 flip flops

Master Slave.

 Here, one clock pulse is divided into 2 halves
first half → +ve edge
second half → -ve edge




The +ve edge goes from low to high.
The -ve edge goes from high to low.

Master will change its state on occurrence of the pulse/edge.

Slave will change its state on the occurrence of the -ve pulse/edge.

Block Diagram

 

logic circuit Master

Slave

